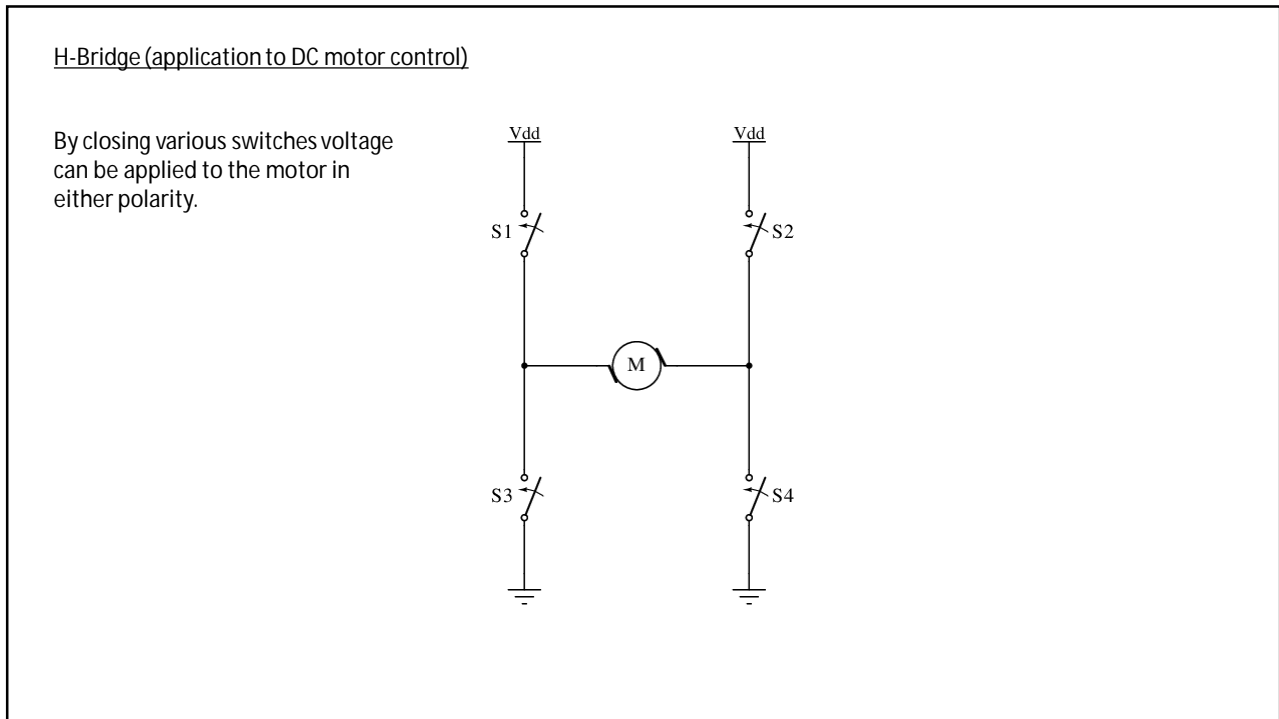


1




2

H-Bridge (application to DC motor control)

By closing various switches voltage can be applied to the motor in either polarity.

 But switches are not enough. The motor is an inductive load (has coils of wire). Thus you **MUST** incorporate flyback diodes.



3


H-Bridge (application to DC motor control)

To run the motor in one direction, say clockwise, close S1 and S4.

To run the motor in the other direction, say counterclockwise, close S2 and S3.

To allow the motor to coast, open all four switches.

 To brake the motor, close S3 and S4 (or alternatively, close S1 and S2).



4


H-Bridge (application to DC motor control)

To run the motor in one direction, say clockwise, close S1 and S4.

To run the motor in the other direction, say counterclockwise, close S2 and S3.

To allow the motor to coast, open all four switches.

 To brake the motor, close S3 and S4 (or alternatively, close S1 and S2).



5


H-Bridge (application to DC motor control)

To run the motor in one direction, say clockwise, close S1 and S4.

To run the motor in the other direction, say counterclockwise, close S2 and S3.

To allow the motor to coast, open all four switches.

 To brake the motor, close S3 and S4 (or alternatively, close S1 and S2).



6


H-Bridge (application to DC motor control)

To run the motor in one direction, say clockwise, close S1 and S4.

To run the motor in the other direction, say counterclockwise, close S2 and S3.

To allow the motor to coast, open all four switches.

 To brake the motor, close S3 and S4 (or alternatively, close S1 and S2).



7


H-Bridge (application to DC motor control)

To run the motor in one direction, say clockwise, close S1 and S4.

To run the motor in the other direction, say counterclockwise, close S2 and S3.

To allow the motor to coast, open all four switches.

 To brake the motor, close S3 and S4 (or alternatively, close S1 and S2).



Warning:
Incorrect switching can
cause a short!

8

H-Bridge (application to DC motor control)

From microcontroller

H-bridge controller (Combinational logic in hardware.)

DIR S1 S2 S3 S4

Brake

PWM

Vdd

Vdd

M

S1

S2

S3

S4

Warning: Incorrect switching can cause a short!

To prevent a short, combinational logic (NOT SOFTWARE) is commonplace.

Inputs			Outputs				Result
Dir	Brake	PWM	S1	S2	S3	S4	
0	0	0	open	open	open	open	Coast
0	0	1	close	open	open	close	Fwd
0	1	0	open	open	open	open	Coast
0	1	1	open	open	close	close	Brake
1	0	0	open	open	open	open	Coast
1	0	1	open	close	close	open	Rev
1	1	0	open	open	open	open	Coast
1	1	1	open	open	close	close	Brake

Never drive H-bridge switches directly from a microcontroller. Physical destruction, maybe even fire, is assured due to software bugs and crashes.

Microcontroller produces Dir, Brake, PWM
No matter what it produces the H-bridge cannot short out the power supply.

9

SPEEDING UP $\frac{dI_L}{dt}$ WITH A FLYBACK DIODE IS USED

REGULAR DIODE $i_D = I_S (e^{\frac{V_D}{nV_T}} - 1)$

USE SERIES RESISTOR -5V SHORTENS THE $\frac{L}{R}$ TIME CONSTANT WHEN SW. IS OPEN BUT AT A COST OF RAISING THE VOLTAGE ACROSS THE SWITCH - NEED A BETTER SWITCH

USE A ZENER DIODE eg. $V_Z = -10V$ CHANGES EXP. DECAY TO A CONSTANT RAMP. WHICH IS FASTER FOR A GIVEN VOLTAGE ACROSS THE SWITCH

TYPICALLY A REGULATOR TO GIVE 12V FROM 15V

USE A HIGHER VOLTAGE SUPPLY - REQUIRES SW IN NEG. SIDE - GIVES CONSTANT RAMP

5V ZENER

12V

15V

12V

15V

15V

12V

15V

10


POSITION ENCODERS — TO SENSE LINEAR OR ANGULAR POSITION

RELATIVE POSITION — A SIGNAL FOR EVERY X DEGREES OF ROTATION
(SOME OTHER MECHANISM IS USED ONE TIME TO EST. ABS. POSITION)

ABSOLUTE POSITION — A MULTI-BIT VALUE FOR EACH POSITION

RELATIVE POSITION

SENSOR NEAR TOOTH = 1
OTHERWISE 0



14 TITS
EXAMPLE
A SENSOR
SIGNAL EVERY
 $\frac{1}{8}$ OF A TURN


TOO SENSITIVE TO VIBRATION
IF YOU STOP ON A BOUNDARY
VIBRATION CAN CAUSE FALSE COUNTS.
(TOO SIMPLE FOR ACTUAL USE
UNDER ANY CONDITION)

RESOLUTION CAN BE
 $\frac{360^\circ}{\# \text{ EDGES}} = \frac{360^\circ}{2 \times \# \text{ TEETH}} = \frac{360^\circ}{2 \times 4} = 45^\circ$

11

QUADRATURE ENCODER POPULAR

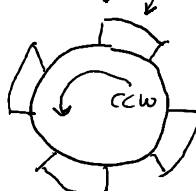SENSOR #1
SENSOR #2
LOCATED 90 ELECTRICAL DEGREE AWAY FROM SENSOR #1 (NOW 22.5° RESOLUTION)



ALTERNATIVE LOCATION FOR SENSOR #2

CCW

SENSOR #1

SENSOR #2

RESOLUTION = $\left(\frac{4 \times \# \text{ OF TEETH}}{360^\circ \text{ MECH.}} \right)^{-1}$

A = 0
ROTATION = 0 RELATIVE TO THE ILLUSTRATION ABOVE

DETECTING DIRECTION OF ROTATION


CCW
SENSOR #1 L → H AND #2 = H1
SENSOR #2 H → L AND #1 = H1
SENSOR #1 H → L AND #2 = L0
SENSOR #2 L → H AND #1 = L0

CW
#1 H → L AND #2 = H1
#2 H → L AND #1 = L0
#1 L → H AND #2 = L0
#2 L → H AND #1 = H1


CW ROTATION TIME →

SENSOR THAT TRANSITIONS → POSITION INFO.
SENSOR THAT DOES NOT TRANSITION → DIR
USE A LOOK-UP TABLE TO DECODE
BOTH SENSORS NEED TO BE READ SIMULTAN...

12

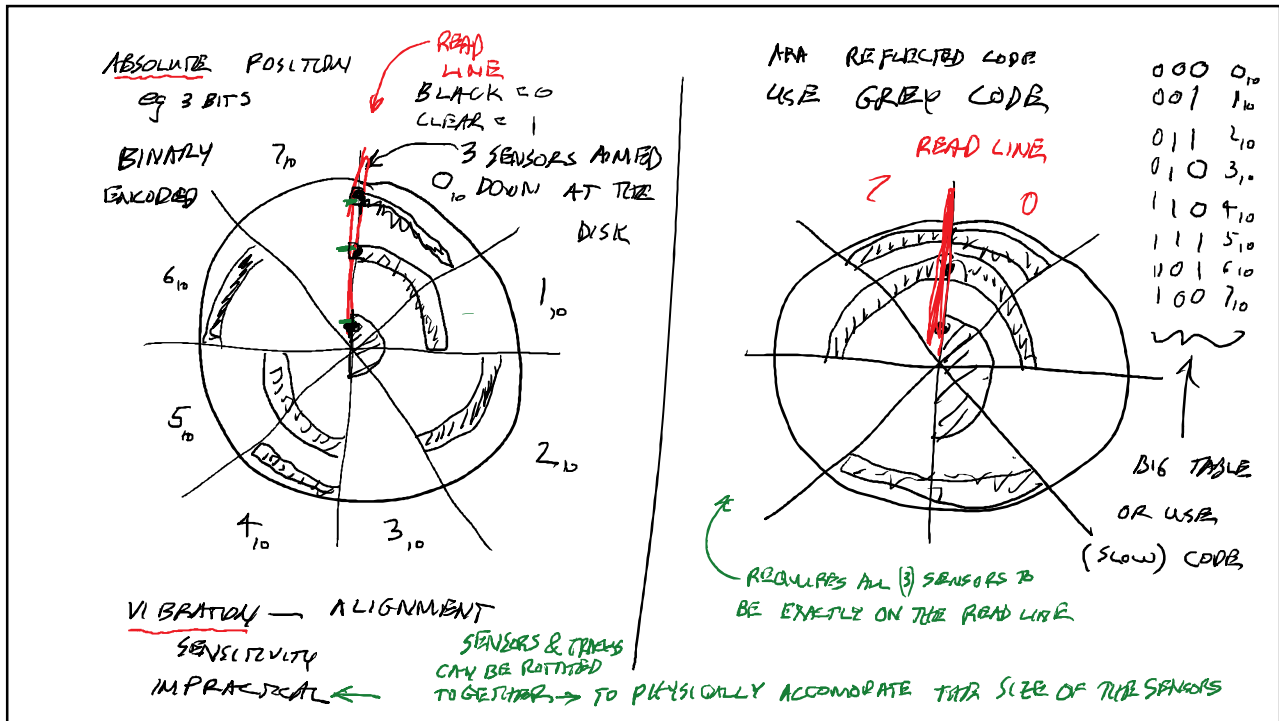

13

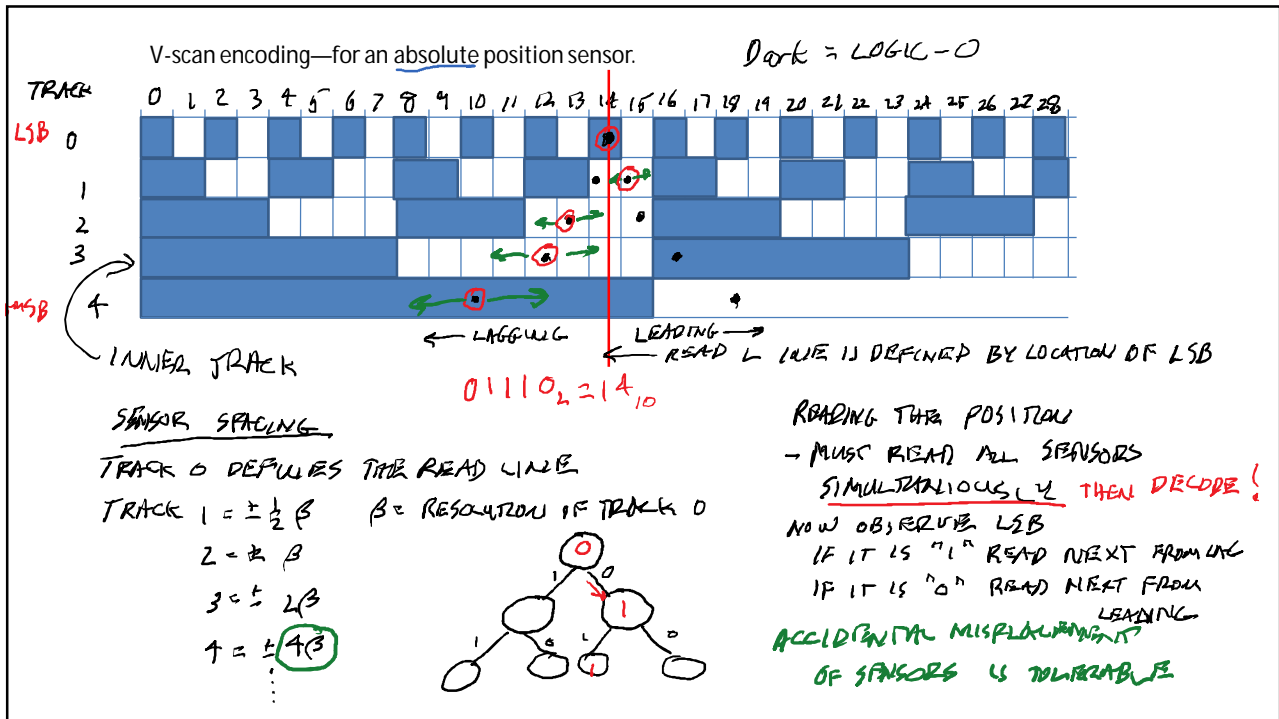

14

U-scan encoding—Same as V-scan except at some point the sensor spacing stops increasing.

eg

TRACK	SPACING
0	0
1	$\pm \frac{1}{2} \beta$
2	$\pm \beta$
3	$\pm 2\beta$
↑	$\pm 2\beta$
↓	$\pm 2\beta$
↓	$\pm 2\beta$
	...
	...
	...


U SCAN UP TO THIS POINT

U SCAN

CALLLED "U-SCAN"


MULTIPLE TURN SCANNING
IS POSSIBLE USING GEAR MECHANISMS

15

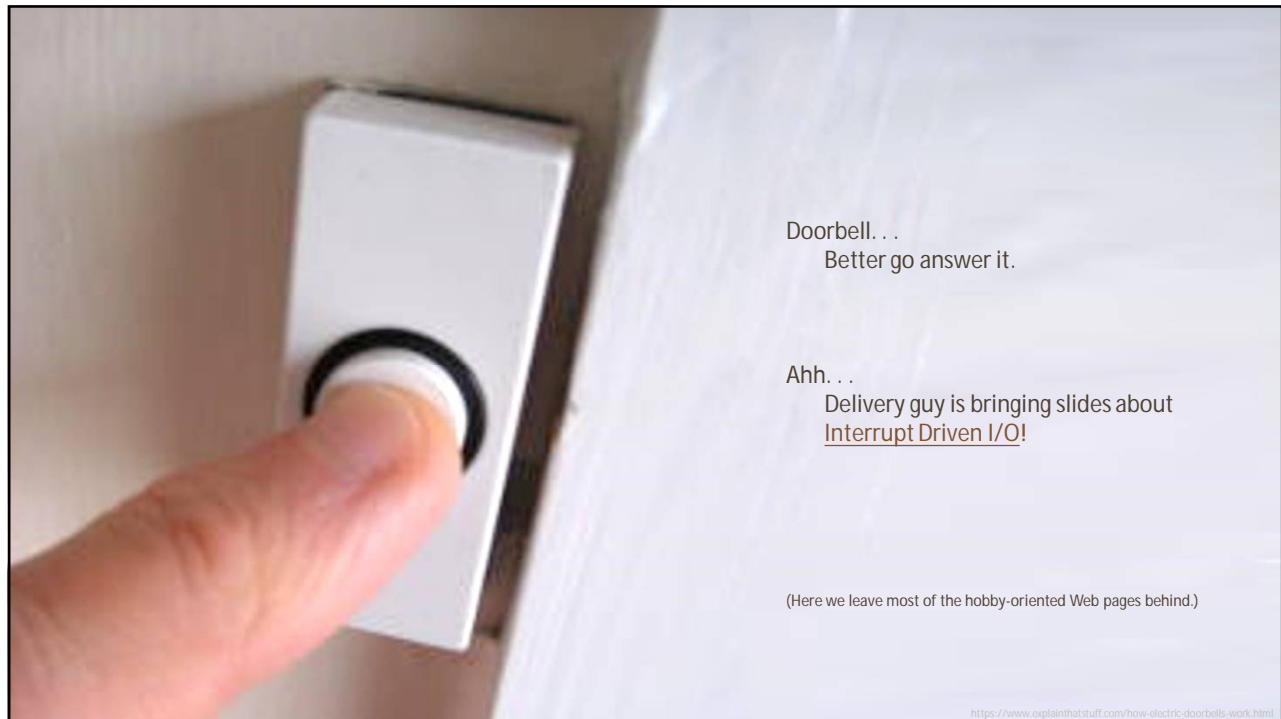

16

Words from the Arduino Forum:

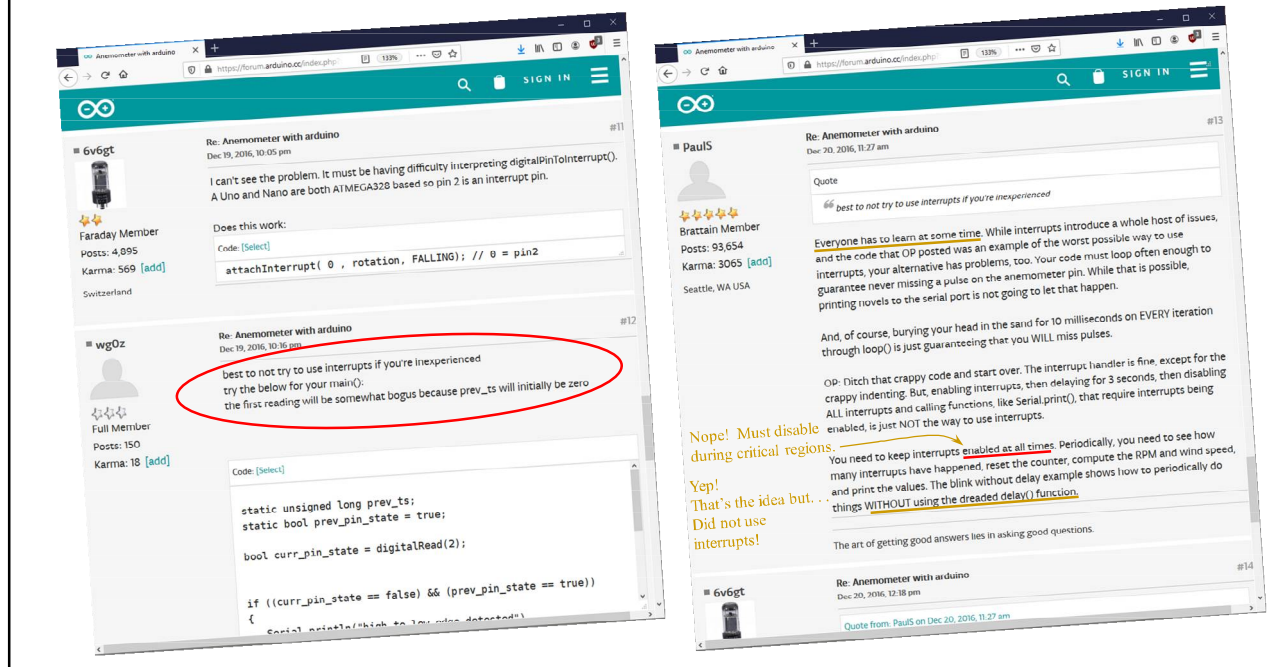

17

How can the port be controlled? How is I/O accomplished with this hardware?

SUMMARY SLIDE

It is a two-step process

- 1.) Setup: place bits in various control registers to establish . . .
 - direction of I/O, input or output
 - if input, and no connection to it, default high (enable pull up resistor), or default low (if available), or random
 - if output, what is the initial output before the first write after power-up?, 1, 0 or X

This slide repeated from 1/17

- 2.) Do the actual I/O. There are various strategies

- a.) **Blind-cycle**: Just do it immediately as the code runs. Not in coordination with the I/O device. (Ready or not, hear I come!)
 - Gadfly: an annoying person (among other meanings)
- b.) **Busy-waiting** (aka **gadfly I/O**): Use a status bit to check the I/O device before reading or writing to it. Result: while I/O device is busy, CPU needs to wait and monitor, hence the name. (The CPU is analogous to kids in the back seat, "Are we there yet? Are we there yet? Are we there yet? . . ." The kids don't do homework while waiting, they busy themselves only with the pestering question.)
- c.) **Periodic polling**: Similar to Busy-waiting, but CPU may work on other threads of code while waiting on a busy I/O device. (Requires a timer interrupt—i.e. requires additional hardware.) (The kids do homework while waiting. Every five minutes a bell rings and they ask the question.)
- d.) **Interrupt driven**: The I/O device has a method in hardware to request I/O service. (The kids stick to their homework until told that they have arrived at their destination.)
- e.) **Direct Memory Access**: The I/O device takes over the CPU bus and writes directly into memory without CPU supervision. (The kids are not in the car!)

18

The agenda—understanding interrupt-driven I/O (and by extension, multitasking)

An example to give some context

Memory capabilities needed for subroutines (functions, procedures, interrupts, are types of subroutines)

Sources of interrupts including counter-timer systems

Advantages of using interrupt-driven I/O—so obvious this section is hardly needed.

- Alternatives to interrupt driven I/O are gadfly (uncontrolled—annoying) I/O or various polling techniques, all of which waste processor cycles prodigiously.
- Interrupts are foundational to object-oriented programming
- Many embedded systems that use interrupts have very little other code to run!

Risks of interrupt-driven I/O

- density limit
- latency and resolution limits
- interval restrictions
- critical regions in code
- deadlock

19

The agenda—understanding interrupt-driven I/O (and by extension, multitasking)

An example to give some context

Memory capabilities needed for subroutines (functions, procedures, interrupts, are types of subroutines)

Sources of interrupts including counter-timer systems

Advantages of using interrupt-driven I/O—so obvious this section is hardly needed.

- Alternatives to interrupt driven I/O are gadfly (uncontrolled—annoying) I/O or various polling techniques, all of which waste processor cycles prodigiously.
- Interrupts are foundational to object-oriented programming
- Many embedded systems that use interrupts have very little other code to run!

Risks of interrupt-driven I/O

- density limit
- latency and resolution limits
- interval restrictions
- critical regions in code
- deadlock

20

120 Vrms, 60 Hz

19:1

RD BK RD

330 Ω

4.8 V

1 k Ω

Arduino +5V pin

Digital I/O pin 2

Arduino GND pin

Tek

Trig'd

M Pos: 0.000s

TRIGGER

Edge Video

Slope Rising

Source CH1

Mode Auto

Coupling DC

CH1 2.00V CH2 2.00V M 5.00ms CH1 / 2.32V

```

#define NOT_AN_INTERRUPT -1 //Required due to
int led_pin = 13;
int inter_pin = 2;
volatile int pulse30Hz = LOW;

/* The Interrupt Service Routine (this one is
 * Notice that this is placed before the setup
 * All this does is toggle pulse30Hz every time
 * This routine is called every time inter_pin
 * It could be programmed to do more, such as
void mains_isr() {
  if (pulse30Hz == LOW) {
    pulse30Hz = HIGH;
  }
  else {
    pulse30Hz = LOW;
  }
  digitalWrite(led_pin, pulse30Hz);
}

void setup() {
  pinMode(led_pin, OUTPUT);
  digitalWrite(inter_pin, LOW); // Disable int
  attachInterrupt(digitalPinToInterrupt(inter_p
}

void loop() {
  // There is nothing to do here!
}
    
```

23

120 Vrms, 60 Hz

19:1

RD BK RD

330 Ω

4.8 V

1 k Ω

Arduino +5V pin

Digital I/O pin 2

Arduino GND pin

Tek

Trig'd

M Pos: 0.000s

TRIGGER

Edge Video

Slope Rising

Source CH1

Mode Auto

Coupling DC

CH1 2.00V CH2 2.00V M 5.00ms CH1 / 2.32V

```

#define NOT_AN_INTERRUPT -1 //Required due to a bug in the IDE (may be fixed by how)
int led_pin = 13;
int inter_pin = 2;
volatile int pulse30Hz = LOW;

/* The Interrupt Service Routine (this one is named "mains_isr")
 * Notice that this is placed before the setup() routine.
 * All this does is toggle pulse30Hz every time it is called write this out to led_pin.
 * This routine is called every time inter_pin goes HIGH, as specified in setup
 * It could be programmed to do more, such as increment a counter.
void mains_isr() {
  if (pulse30Hz == LOW) {
    pulse30Hz = HIGH;
  }
  else {
    pulse30Hz = LOW;
  }
  digitalWrite(led_pin, pulse30Hz);
}

void setup() {
  pinMode(led_pin, OUTPUT);
  digitalWrite(inter_pin, LOW); // Disable internal pull-up resistor
  attachInterrupt(digitalPinToInterrupt(inter_pin), mains_isr, RISING);
}

void loop() {
  // There is nothing to do here!
}
    
```

24